

Printed Pages : 4



EAG-401

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 180408

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. IV) THEORY EXAMINATION, 2014-15

ELECTRICAL CIRCUITS & MACHINE

Time : 3 Hours]

[Total Marks : 100

Note : Attempt all questions.

1 Attempt any four parts of the following : **5×4=20**


- (a) Explain the double revolving field theory.
- (b) What are the advantages of low power factor? Mention some methods of improving power factor.
- (c) Explain two wattmeter method of measurement of three phase power with the help of circuit and phase diagram?
- (d) Explain the principle of operation of a dc motor.
- (e) What is the need of using starter in :
 - (i) Three-phase induction motor
 - (ii) Single-phase induction motor

2 Attempt any four parts of following : $5 \times 4 = 20$

- (a) Mention and explain various electric safety rules.
- (b) Describe with neat sketch, the star delta starting of three phase induction motor.
- (c) A 20 V series motor is developing a torque of 10 N-m when running at 1200 rpm. The total armature and series field resistance is 0.6Ω . Calculate the motor current.
- (d) Why improvement of power factor is needed? Explain.
- (e) Explain voltage control in 3-phase induction motor. What type of load is more suitable for this method?

3 Attempt any two parts of the following : $10 \times 2 = 20$

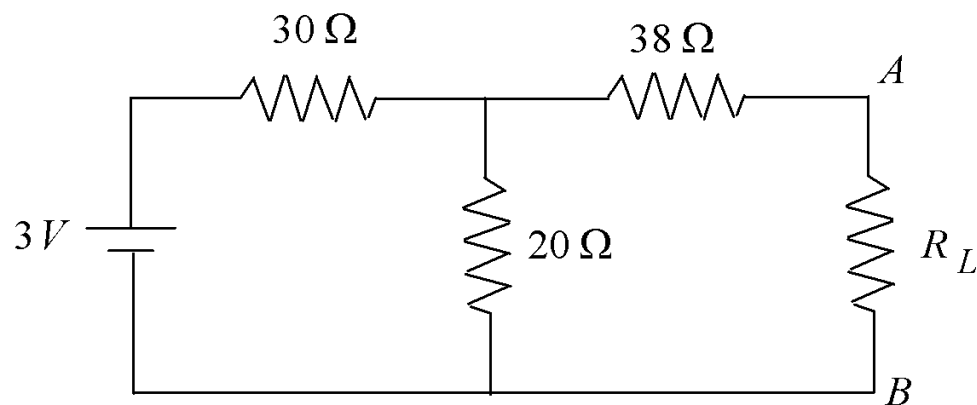- (a) Explain the Thevenin's, Norton's superposition power transfer in detail
- (b) Explain maximum power transfer theorem. And find the value of load resistance R_L in the given diagram and determine the maximum power transferred.



- (c) Write short note on :
- (i) Hysteresis and eddy current loss
 - (ii) Leakage resistance
 - (iii) Voltage regulation
 - (iv) EMF and torque equation

4 Attempt any two parts of the following : **10×2=20**

- (a) Describe the construction, operation, equivalent circuit and phasor diagram for a poly phase induction motor.
- (b) The following results were obtained on 50 kVA, 2400/120 Volt transformer.

Open circuit test, instruments on L.V. side

Wattmeter reading =396W

Ammeter reading =9.65A

Voltmeter reading=120V

Short circuit test, instruments on H.V. Side

Wattmeter reading =810W

Ammeter reading =20.8A

Voltmeter reading=92V

Find :

- (i) The equivalent circuit constant
- (ii) The efficiency at full load, 0.8 pf lagging.
- (iii) The approximate voltage regulation

- (c) Why starters are necessary for starting of three-phase induction motors? Describe with the help of diagram, the rotor resistance starter for 3-phase slip-ring induction motor.

5 Attempt any two parts of the following : **10×2=20**

- (a) What do you understand by instantaneous and average power, power factor, reactive and apparent power? Describe in detail.
- (b) Explain procedure for transforming Delta connected network into star connected network and star to Delta transformation. Derive formula in detail.
- (c) A long shunt compound generator supplies a load of 20 kW at 500 V. The armature, series and shunt field resistance are 0.1Ω , 0.05Ω and 100Ω respectively. Calculate the EMF and also draw the schematic circuit.
-