



(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 130404

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. IV) THEORY EXAMINATION, 2014-15 NETWORK ANALYSIS AND SYNTHESIS

Time : 3 Hours]

[Total Marks : 100

- Note:** (1) Attempt all questions.
(2) All questions carry equal marks.

- 1 Attempt **any four** parts of the following: **5x4=20**
- (a) Show that f-cutset and f-loop matrix are orthogonal to each other.
 - (b) Draw the oriented graph of network given in fig1. & write the incidence & reduced incidence matrix

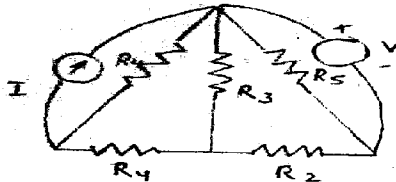


Fig-1

- (c) Define with suitable example: (i) Tree (ii) Planar graph (iii) Incidence matrix (iv) Twigs (v) Chord.
- (d) Write the principle of duality & draw the dual of the network given in fig2.

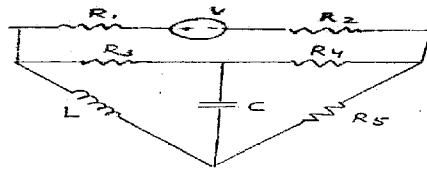


Fig-2

- (e) For the network shown in fig3. draw the oriented graph, select a suitable tree and obtain the fundamental cut-set matrix. Determine the node equations and find v .

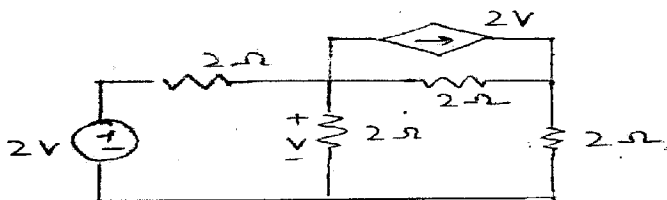


Fig-3

- (f) The fundamental cut-set matrix is given below. Draw the oriented graph of the network.

2 Attempt **any two** parts of the following: **10x2=20**

- (a) In the network given in fig4. two voltage sources act on the load impedance connected to the terminals a and b. If the load is variable in both reactance and resistance what load Z_L will receive the maximum power? Use maximum power transfer theorem.

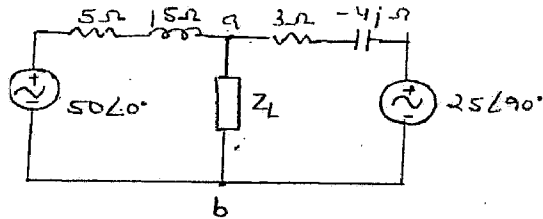


Fig-4

- (b) In the network given in Fig.5. find current through inductor connected across a and b using Thevenin theorem.

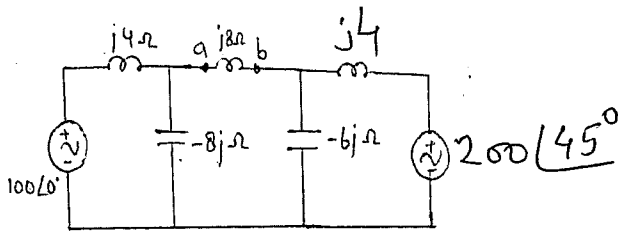


Fig-5

- (c) Find the value of source E_2 using Tellegen's theorem if the power absorbed by E_2 is 120 W in fig.6.

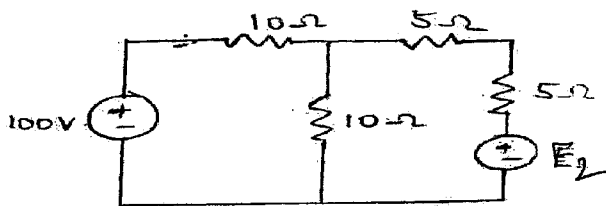


Fig-6

3 Attempt **any two** parts of the following: **10x2=20**

- (a) Obtain the expression for the current in a series RL circuit connected to a dc voltage V for $t > 0$. Assume initial current through inductor as zero. Also draw the response graph for the current through inductor and from the graph define time constant of the circuit.
- (b) In the network shown in fig7. the switch K is opened at $t=0$. Solve for V , dv/dt and d^2v/dt at $t=0^+$.

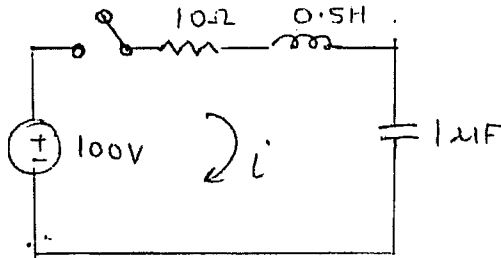


Fig-7

- (c) Obtain current $i(t)$ for $t \geq 0$ using time domain approach for the network given in fig.8. The switch is closed at $t=0$.

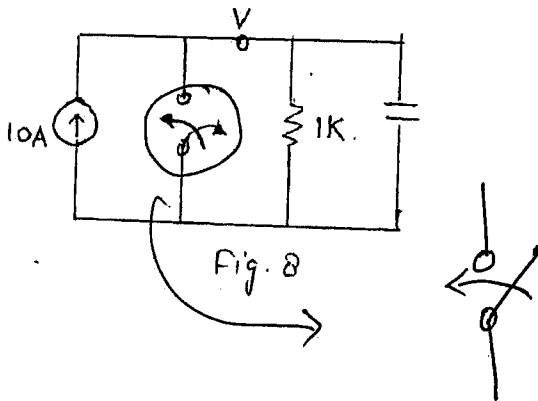


Fig-8

4 Attempt **any two** parts of the following : **10x2=20**

- (a) The ABCD parameters of a two port n/w are $A=2$, $B=5$, $C=1/3$, $D=4/3$, Determine z , y & h -Parameters.

- (b) Find the transmission parameters for the network shown in fig9. considering two networks connected in cascade.

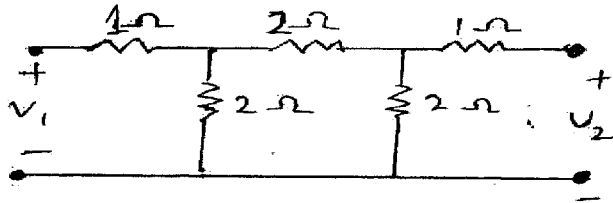


Fig-9

- (c) (i) Find the number of closed loop poles in the left half s-plane for a system whose characteristic equation is $S^4 + 2S^3 + 3S^2 + 4S + 5 = 0$

Comment on stability of the system.

- (ii) What are poles and zeroes? How does the location of poles in the s-plane affect the system stability? Explain.

5 Attempt **any two** parts of the following: **10x2=20**

- (a) What is the difference between active and passive filters? Design a constant K type bandpass filter section to be terminated in 600Ω resistance having cut-off frequencies of 2kHz and 5kHz.
- (b) Synthesize (i) $Z(s) = (s+1)(s+3)/[(s+6)s]$ in cauer - I form. (ii) $Z(s) = (s+5)/[(s+1)(s+6)]$ in Foster's - II form.
- (c) Test whether given polynomial is positive

real function or not. $Z(S) = \frac{S^2 + 2S + 25}{S + 4}$.
