



(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 121406

Roll No.

--	--	--	--	--	--	--	--	--	--

B. Tech.

(SEM. IV) THEORY EXAMINATION, 2014-15
NETWORK ANALYSIS & SYNTHESIS

Time : 3 Hours]

[Total Marks : 100

Note : Attempt all questions.

- 1 Attempt **any TWO** parts of the following: **10×2=20**
- (a) Explain the followings matrices taking a suitable example:
 - (i) Reduced Incidence Matrix
 - (ii) Basic Cutset Matrix
 - (iii) Basic Tieset Matrix
 - (b) Derive the KCL and KVL using network graph variables.
 - (c) Explain the concept of duality. Find the dual of the network shown in figurel.

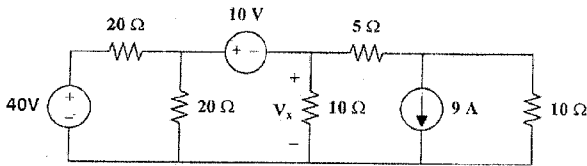


Fig. 1

- 2 Attempt **any FOUR** parts of the following. **5×4=20**
- (a) Find the current I and voltage V_{ab} in figure2.



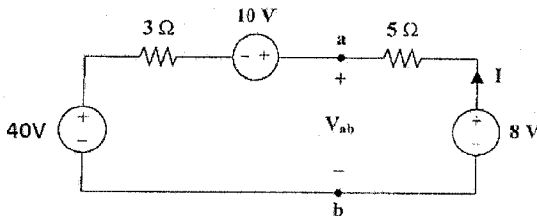


Fig. 2

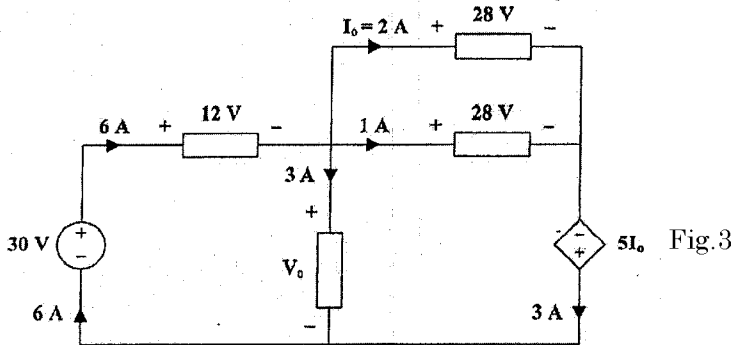
- (b) Derive the maximum power transfer theorem for the case when the source impedance is complex and the load is variable with its power factor being unity.
- (c) Find the voltage V_o in figure 3 below.



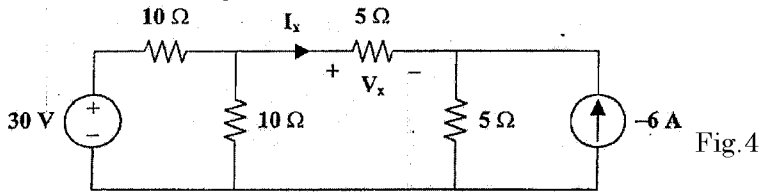- (d) Find the current I_x through the 5 ohm resistor using Thevenin's theorem in figure 4.




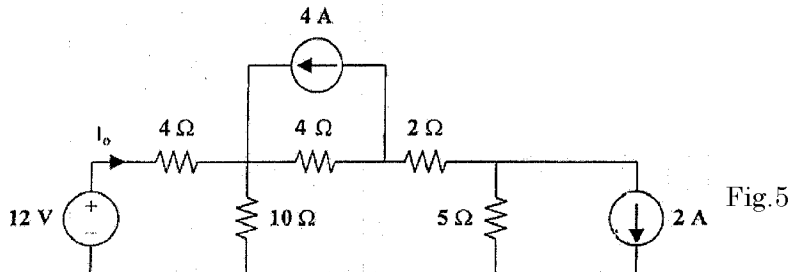- (e) Find the current I_o using source transformation in figure 5.




- (f) State and prove the Tellegen's theorem.

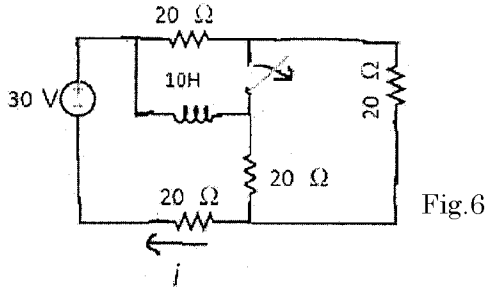3. Attempt **any TWO** parts of the following. **10×2=20**
 (a) (i) In the circuit shown in figure 6, the switch is kept closed for a long time and is then opened at $t=0$.




Find the values of current i just before opening the switch ($t = 0^-$) and just after opening the switch ($t = 0^+$).

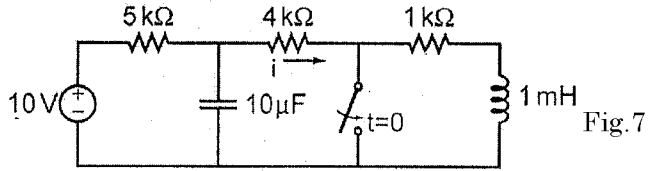
- (ii) In the figure7 shown, the ideal switch has been open for a long time. If it is closed at $t=0$, then find the magnitude of current (in mA) through the $4k\Omega$ resistor at $t=0^+$?



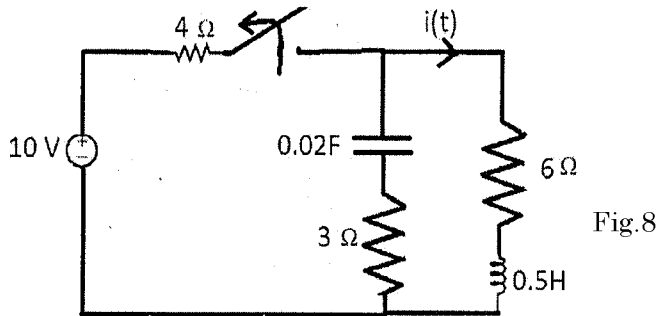
- (b) Find the expression of the current $i(t)$ in the circuit of figure 8 assuming that the switch is opened at $t=0$, the steady state having already reached before that.



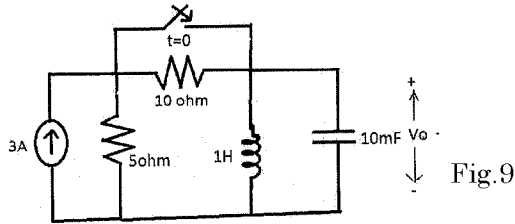- (c) Find the voltage V_o in the circuit of figure 9. The switch was open for a long time before it was closed at $t=0$.



- 4 Attempt **any FOUR** parts of the following: **5×4=20**
- Write the necessary conditions for the existence of transfer functions giving a suitable example.
 - What is meant by reciprocal and symmetric networks? Explain with the help of an example.
 - Derive the condition of reciprocity and symmetry for h-parameters.
 - Prove that if two 2-port networks are connected in cascade, the transmission parameter matrix of the composite two port network is the product of the two individual transmission parameter matrices.
 - Find the Y and h parameters of the network shown in figure 10.

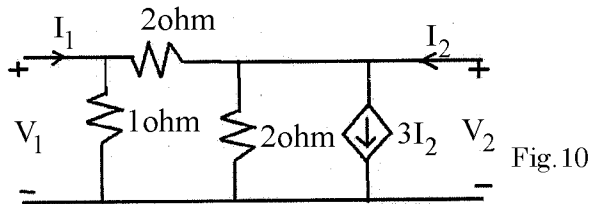

- (f) Prove that the star delta conversion does not bring any change in the Z parameter matrix for the case of a resistive network.
- 5 Attempt **any TWO** parts of the following. **10×2= 20**

(a) Given
$$Z(s) = \frac{10(s^2 + 4)(s^2 + 6)}{s(s^2 + 5)}$$

- Find the Foster I and Cauer II forms of network.
- Explain the properties of positive real functions, LC functions and R-L functions.
- What is image parameter? Derive its expression. What are active and passive filters? Explain the advantages of active filters.