

Correction in EEE602

POWER ELECTRONICS

Date: 15-05-2015

Evening Shift

Corrections:

Q3(a). A single phase half controlled bridge operated from the 230V, 50 HZ mains feed a resistive load of 100 ohm. If the firing angle is 60° , calculate

- i. Average output voltage**
- ii. rms output voltage**
- iii. Total output power**
- iv. DC output power**
- v. Load current at instant of turn on**

Q3(c). Discuss the working of 1 full wave ac-dc converter taking into account the effect of source inductance. Draw the output voltage waveform for firing angle of 30° .

Q5(b). Explain operation of a 3 bridge inverter employing 120° mode of operation. Draw waveforms of phase voltages and any one line voltage assuming star connected resistance load.